



Province of the  
**EASTERN CAPE**  
EDUCATION

**NATIONAL  
SENIOR CERTIFICATE**

**GRADE 11**

**NOVEMBER 2012**

**ELECTRICAL TECHNOLOGY  
MEMORANDUM**

**MARKS: 200**

---

This memorandum consists of 11 pages.

---

**QUESTION 1: TECHNOLOGY, SOCIETY AND THE ENVIRONMENT**

- 1.1
- A sound knowledge of electronics to ensure the best possible technical design to produce a quality product. ✓
  - A sound knowledge in handling financial matters to ensure a well-run sustainable business. ✓
  - (ANY RELEVANT ANSWER WILL BE ACCEPTED) (2)
- 1.2
- Switch off all the unused electrical appliances and lights. ✓
  - Do not use your dishwasher, laundry equipment, coffee maker or other home heavy appliance after 7 pm. ✓
  - Use microwave oven to cook small quantities of food. ✓
  - Lower your thermostat a degree or two degrees. ✓
  - (ANY RELEVANT ANSWER WILL BE ACCEPTED) (4)
- 1.3
- Cell phone. ✓
- Positive: Contact with family and friends any time you want. ✓
- Negative: Expose to pornography on phones. ✓
- (ANY RELEVANT ANSWER WILL BE ACCEPTED) (3)
- 1.4 Communication skill (1)
- [10]**

**QUESTION 2: TECHNOLOGICAL PROCESS**

- 2.1
- Identify the problem. ✓
  - Investigate. ✓
  - Do research. ✓
  - Assess. ✓
  - Process. ✓
  - ANY THREE (3)
- 2.2
- 2.2.1 Design and build an electronic warning sign to alert the traffic about cyclists and athletes. ✓✓✓ (3)
- 2.2.2
- The device should be portable. ✓
  - It should be easy to use. ✓
  - It should be easy to maintain. ✓
  - It should flash colourful lights visible to motorists. ✓ (4)
- [10]**

**QUESTION 3: OCCUPATIONAL HEALTH AND SAFETY**

- 3.1 Safety is the main consideration behind all rules and regulations contained in the CODE of PRACTICE for the wiring of electrical installation.  $\sqrt{\sqrt{}}$  (2)
- 3.2
- There should be no slippery surface.  $\sqrt{}$
  - Tidy workshop.  $\sqrt{}$
  - (ANY RELEVANT ANSWER WILL BE ACCEPTED) (2)
- 3.3
- There should be enough space between the machines.  $\sqrt{}$
  - Poorly ventilated work area.  $\sqrt{}$
  - (ANY RELEVANT ANSWER WILL BE ACCEPTED) (2)
- 3.4
- Stand firmly when working with a portable drilling machine.  $\sqrt{}$
  - Remove the chuck key from the chuck after loosening or tightening the bit.  $\sqrt{}$  (2)
- 3.5 Ensure the main supply has been switched off.  
Use a wooden or non-conductive object to release/remove him/her from the conductor.  $\sqrt{\sqrt{}}$  (2)

**[10]****QUESTION 4: INSTRUMENTS**

- 4.1 8 div =  $360^\circ$  One full cycle  
1 div =  $45^\circ$   
The waves are  $45^\circ$  apart  
I lags V by  $45^\circ\sqrt{\sqrt{}}$  (2)
- 4.2 Volt/div = 10 V  
 $V_{\max} = \text{No. of div} \times \text{volt /div}$   
=  $3 \times 10\sqrt{}$   
= 30 V $\sqrt{}$  (2)
- 4.3 T = time /div  $\times$  No. of div $\sqrt{}$   
=  $2,5 \text{ ms} \times 8\sqrt{}$   
= 20 ms $\sqrt{}$  (3)
- 4.4  $V_{\text{RMS}} = 0,707 \times V_{\max} \sqrt{}$   
=  $0,707 \times 30\sqrt{}$   
= 21,21 V  $\sqrt{}$  (3)

**(3)**  
**[10]**

**QUESTION 5: PRINCIPLE OF SINGLE-PHASE GENERATION**

- 5.1
- As the conductor loop is rotated through the magnetic field, each of the two sides of the loop move through the magnetic field cutting the magnetic lines of flux. ✓
  - This action induces an alternating voltage across the conductor loop. ✓ (2)
- 5.2 When the loop is perpendicular to the magnetic field. ✓? (1)
- 5.3  $i = 12 \sin 314t$
- 5.3.1  $I_{ave} = 0,637 \times I_{max}$   
 $= 0,637 \times 12 \sqrt{}$   
 $= 7,64 \text{ A } \sqrt{}$  (2)
- 5.3.2  $T = 1,5 \text{ ms.}$   
 $i = 12 \sin 314t$   
 $= 12 \sin 314^\circ \times 1,5 \times 10^{-3} \times 57,3 \sqrt{}$   
 $= 5,45 \text{ A } \sqrt{}$  (3)
- 5.4 5.4.1 230 V rms  
 $V_{rms} = 0,707 \times V_{max}$   
 $V_{max} = \frac{230}{0,707} \sqrt{}$   
 $= 325,32 \text{ V } \sqrt{}$  (2)
- 5.4.2  $V_{ave} = 0,637 \times V_{max}$   
 $= 0,637 \times 352,32 \sqrt{}$   
 $= 207,23 \text{ V } \sqrt{}$  (2)
- 5.4.3  $T = \frac{1}{F} \sqrt{}$   
 $= \frac{1}{50} \sqrt{}$   
 $= 20 \text{ ms } \sqrt{}$  (3)

**[15]**

**QUESTION 6: RLC CIRCUITS**

6.1 Impedance of the circuit is the total opposition a circuit offers to the flow of current. It depends entirely to the frequency of the supply when connected to the alternating voltage supply.  $\checkmark\checkmark\checkmark$  (3)

6.2 6.2.1 Nothing is going to happen as the resistor and the frequency have no relationship.  $\checkmark$  (1)

6.2.2 Capacitive reactance will decrease.  $\checkmark$  (1)

6.2.3 Inductive reactance will also increase.  $\checkmark$  (1)

6.3 6.3.1  $X_L = 2\pi fL\checkmark$   
 $= 2 \cdot \pi \cdot 50 \cdot 75 \cdot 10^{-3}\checkmark$   
 $= 23,56 \Omega\checkmark$

$$X_C = \frac{1}{2\pi fC} \checkmark$$

$$= \frac{1}{2 \cdot \pi \cdot 50 \cdot 220 \cdot 10^{-6}} \checkmark$$

$$= 14,47 \Omega\checkmark$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}\checkmark$$

$$= \sqrt{22^2 + (23,56 - 14,47)^2}\checkmark$$

$$= 23,8 \Omega\checkmark \quad (9)$$

6.3.2  $I = \frac{V}{Z}\checkmark$

$$= \frac{24}{23,8}\checkmark$$


$$= 1,01 \text{ A } \checkmark \quad (3)$$

6.3.3  $\theta = \text{Cos}^{-1} (R/Z) \checkmark$

$$= \text{Cos}^{-1} (22/23,8) \checkmark$$

$$= 22,43^\circ\checkmark \quad (3)$$

6.3.4

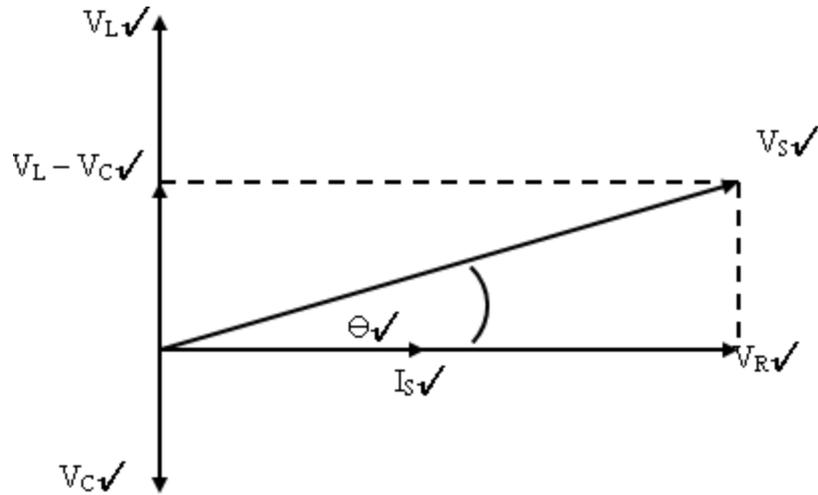

(4)

- 6.4
- $X_L = X_C$ . ✓
  - Impedance is at minimum. ✓
  - Current is at maximum. ✓

(2)

- 6.5
- Radio tuning circuit. ✓
  - Filtering circuit. ✓
  - Oscillating circuit. ✓

(2)

- 6.6 Yes ✓

(1)

**[30]**

### QUESTION 7: SEMI-CONDUCTOR DEVICES

7.1

$$\begin{aligned} \text{Gain} &= \frac{V_{\text{output}}}{V_{\text{input}}} \checkmark \\ &= \frac{3V_{p-p}}{0.02V_{p-p}} \checkmark \\ &= 150 \checkmark \end{aligned}$$

(3)

- 7.2
- Transistor as a switch. ✓
  - Transistor as an amplifier. ✓

(2)

- 7.3 The trigger angle (and so the power available to the load) is controlled by  $R_2$ .  $R_1$  and  $R_2$  form a voltage divider which with  $D_1$  sets up the necessary triggering potential.  $D_2$  is the triggering device which conducts a positive voltage pulse to the gate only once its breakdown voltage of 0.6 V is overcome. By varying  $R_2$  the voltage level at the gate of the thyristor will vary, so changing the trigger angle and therefore the power available to the lamp, changing the brightness of the lamp.

(5)

**[10]**

**QUESTION 8: AMPLIFIERS**

- 8.1
- Common Emitter ✓
  - Common Base ✓
  - Common Collector ✓
- (3)

8.2

$$I_c = \frac{V_{cc}}{R_c}$$

$$R_c = \frac{V_{cc}}{I_c} \checkmark$$

$$R_c = \frac{24V_{dc}}{150 \times 10^{-3}} \checkmark$$

$$R_c = 160 \Omega \checkmark$$

(3)

8.3

$$X_c = \frac{1}{2\pi f C} \checkmark$$

$$C = \frac{1}{2\pi f X_c} \checkmark$$

$$= \frac{1}{2\pi \cdot 100 \times 33} \checkmark$$

$$= 48,23 \times 10^{-6}$$

$$= 48,23 \mu f \checkmark$$

(4)  
[10]

**QUESTION 9: TRANSFORMERS**

- 9.1
- Instrument transformer ✓
  - Power transformer ✓
- (2)

9.2 9.2.1 Transformer may be overloaded. ✓✓

(2)

- 9.2.2
- Oil ✓
  - Air ✓
  - Water ✓
- (3)

9.2.3

$$I_p = S / V_p \checkmark$$

$$= 1\,100\,000 / 11\,000 \checkmark$$

$$= 100 A \checkmark$$

(3)

$$\begin{aligned}
 9.2.4 \quad I_S &= \frac{I_P \cdot V_P \checkmark}{V_S} \\
 &= \frac{100 \times 11000 \checkmark}{230} \\
 &= 4\,782,61 \text{ A} \checkmark \quad (3)
 \end{aligned}$$

- 9.3
- Shell type ✓
  - Core type ✓
- (2)  
[15]

### QUESTION 10: POWER SUPPLY


- 10.1
- Transformer ✓
  - Rectifier ✓
  - Smoothing ✓
  - Regulation ✓
- (4)

10.2 Smoothing the ripples from the rectifier. ✓✓ (2)

10.3 As the input voltage rises above the Zener breakthrough voltage, ✓ the internal resistance of the Zener will lower and allow current to pass through it. ✓ This will result in more current flowing into the base of the transistor, ✓ causing its internal resistance to lower and as a result thereof the voltage over the transistor will lower as well, ✓ thus resetting the output voltage. ✓ (5)

10.4 10.4.1 Electrolytic capacitor ✓ (1)

10.4.2 Photo-diode ✓ (1)

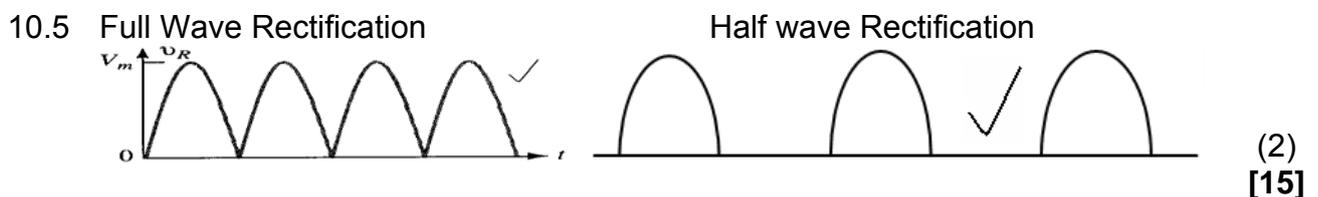


**QUESTION 11: LOGIC CIRCUITS**

11.1 11.1.1 NAND Gate ✓ (1)

11.1.2 NOR Gate ✓ (1)

11.1.3 NOT Gate ✓ (1)

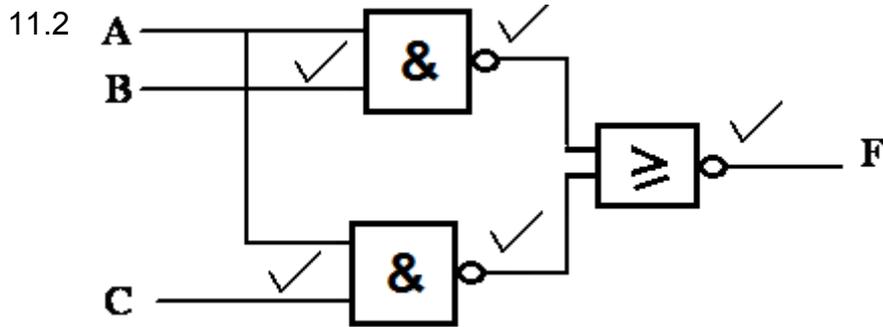

$$F = \overline{\overline{A.B} + \overline{A.C}} \quad (5)$$

11.3

$$\begin{aligned}
 F &= A.B + A.C \\
 &= \overline{\overline{A.B} \cdot \overline{A.C}} \checkmark \\
 &= \overline{\overline{A} \cdot \overline{B} \cdot \overline{A} \cdot \overline{C}} \checkmark \\
 &= \overline{\overline{A} \cdot \overline{B} \cdot \overline{A} \cdot \overline{C}} \checkmark \\
 &= A.B.C \checkmark
 \end{aligned} \quad (4)$$

11.4 11.4.1 1✓ (1)

11.4.2 1✓ (1)

11.4.3 1✓ (1)

- 11.5
- Alarm Systems ✓ (2)
  - Computers ✓ (2)

11.6 11.6.1 X + Y (1)

11.6.2 1 (1)

11.6.3 X (1)


**QUESTION 12: PROTECTIVE DEVICES**

- 12.1 12.1.1 Live in terminal ✓ (1)
- 12.1.2 Live out terminal ✓ (1)
- 12.1.3 Trip switch ✓ (1)
- 12.1.4 Moving contact ✓ (1)
- 12.2 12.2.1 40 A ✓ (1)
- 12.2.2 20 A ✓ (1)
- 12.3 The function of an earth-leakage relay unit is to automatically disconnect an installation or circuit from the supply in the event of a leakage of 20 mA or more flowing to earth. ✓✓ (2)
- 12.4 Advantages of a circuit-breaker compared to that of a fuse:
- In the event of an overload or fault, all poles of the circuit are positively disconnected. ✓
  - The devices are also capable of remote control by push-buttons, by under-voltage release coils, or by earth-leakage relay trip coils. ✓
- (2)
- [10]**

**QUESTION 13: OPERATING PRINCIPLES OF SINGLE-PHASE MOTORS**

- 13.1 13.1.1 Running windings ✓ (1)
- 13.1.2 Auxiliary winding ✓ (1)
- 13.1.3 Starting capacitor ✓ (1)
- 13.1.4 Centrifugal switch ✓ (1)
- 13.2 Capacitor-start induction motor ✓ (1)
- 13.3 To open up at about 75% of operating speed and remove the starting capacitor and starting winding from the supply. ✓✓ (2)
- 13.4 Where a good starting torque is required ✓✓ i.e. motors that will start under load. ✓ (3)
- 13.5 The motor will not automatically start because the two phase effect has not been created. ✓✓ (2)

13.6

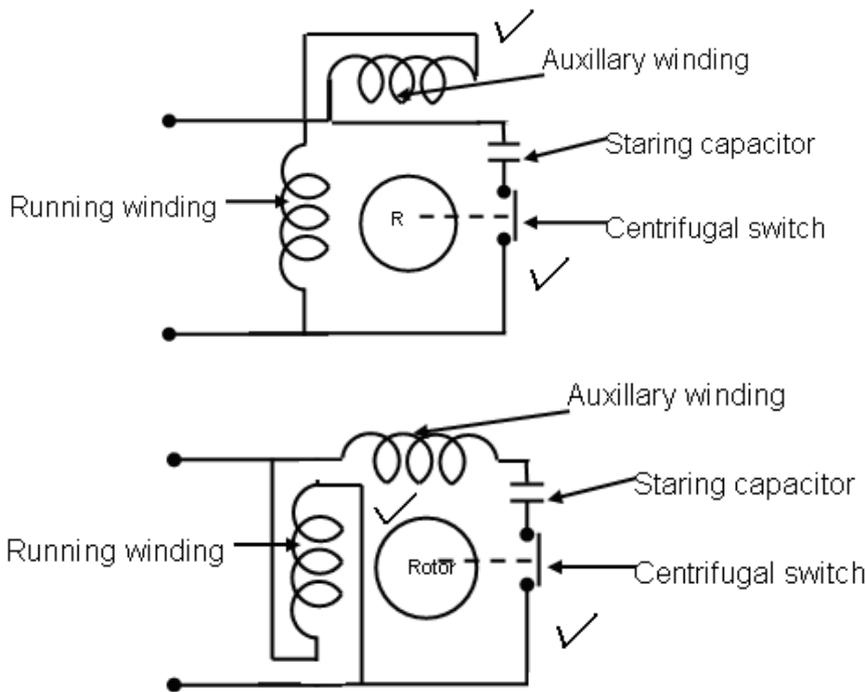


(4)

13.7 The two capacitors create a phase shift between the current in the main winding and the current in the starting winding. ✓✓ This in turn creates a two phase effect in the stator which created a rotating magnetic field that is required to start the motor. ✓✓

(4)

13.8

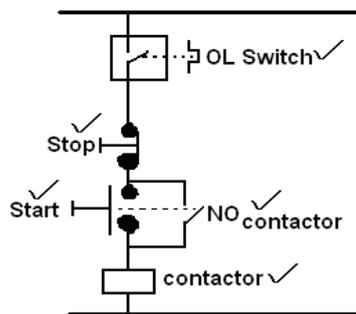

(5)  
[25]

**QUESTION 14: ELECTRONIC COMMUNICATION**

14.1 Modulation is the process of combining the information with the carrier wave. ✓✓

(2)


14.2 Yes

(1)

14.3 The capacitor is acting as a filter, removing the RF and producing an audio signal on the output. ✓

(2)

14.4

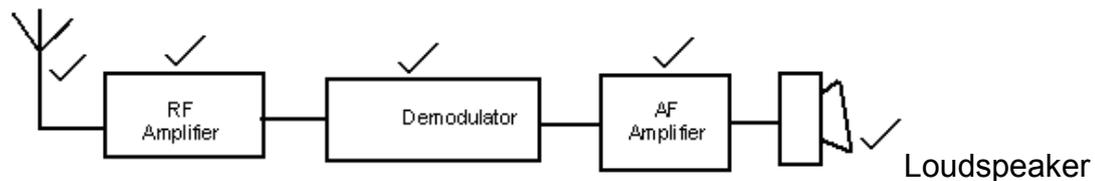

(5)  
[10]

**TOTAL: 200**