



Province of the  
**EASTERN CAPE**  
EDUCATION

**NATIONAL  
SENIOR CERTIFICATE**

**GRADE 12**

**SEPTEMBER 2014**

**ELECTRICAL TECHNOLOGY  
MEMORANDUM**

**MARKS: 200**

---

This memorandum consists of 13 pages.

---

**QUESTION 1: OCCUPATIONAL HEALTH AND SAFETY**

- 1.1 An accident is an unplanned, √ uncontrolled event √ caused by unsafe acts and conditions. √ (3)
- 1.2 No. √ The employee has the right to privacy. √ (2)
- 1.3 • Apply direct pressure or use a pressure bandage. √  
 • Keep the victim calm. √  
 • Keep the bleeding point above the heart level if possible. √  
 • When there is arterial bleeding, pressure may be insufficient, and it may be necessary to use a tourniquet. √  
 • A tourniquet may be used but the tourniquet pressure must be relieved periodically to prevent tissue damage. √ (5)  
**[10]**

**QUESTION 2: THREE-PHASE AC GENERATION**

- 2.1 (The question asked for methods used in South Africa.)  
 • Wind  
 • Solar  
 • Hydroelectric  
 • Pumped storage (Any 2 x 1 √√) (2)
- 2.2 • Copper losses  
 • Iron or core losses  
 • Friction losses  
 • Windage losses (Any 3 x 1 √√√) (3)
- 2.3 Generation process  
 • For three-phase and single phase alternators of similar sizes three-phase will generate more power.  
 • Three-phase can supply power to single and three-phase loads.  
 • Three-phase is cheaper to generate.  
 • Three-phase requires less maintenance.  
 • Three-phase has two connection options, star and delta. (Any 1 x 2√√)

Transmission and distribution process

- Lower currents mean less heat.
- Less heat means fewer losses.
- Lower current means thinner cables can be used reducing costs.
- Pylons required to support thinner cables will require less metal during construction reducing costs.
- A neutral point is available when connected in star.
- Load distribution and phase balancing becomes possible. (Any 1 x 2 √√)

The load

- Three-phase motors are more efficient.
- Three-phase motors have a higher power factor.
- Three-phase motors have a much higher starting torque.
- Three-phase motors do not need additional starting circuitry.
- For three-phase and single phase motors of similar physical sizes, three-phase will produce more power.
- Three-phase can be connected in star or delta. (Any 1 x 2 ✓✓) (6)

$$\begin{aligned}
 2.4 \quad 2.4.1 \quad V_L &= \sqrt{3} \times V_{PH} \checkmark \\
 &= \sqrt{3} \times 240 \checkmark \\
 &= 415,69 \text{ V } \checkmark
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.4.2 \quad S &= \sqrt{3} I_L V_L \\
 I_L &= \frac{S}{\sqrt{3} V_L} \checkmark \\
 &= \frac{15\,000}{\sqrt{3} \times 415,69} \checkmark \\
 &= 20,83 \text{ A } \checkmark
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 2.4.3 \quad P &= \sqrt{3} I_L V_L \cos\theta \checkmark \\
 &= \sqrt{3} \times 20,83 \times 415,69 \times 0,87 \checkmark \\
 &= 13,05 \text{ kW } \checkmark
 \end{aligned}$$

OR

$$\begin{aligned}
 P &= S \cos\theta \\
 &= 15\,000 \times 0,87 \\
 &= 13,05 \text{ kW}
 \end{aligned} \tag{3}$$

**[20]**

**QUESTION 3: THREE-PHASE TRANSFORMERS**

- 3.1 • Identical turns ratios  
 • Identical voltage and current ratings  
 • Identical power ratings  
 • Identical power factor  
 • Identical efficiency  
 • Identical size

(Any 3 x 1 ✓✓✓) (3)

3.2 3.2.1  $V_{L(\text{SECONDARY})} = V_{L(\text{LOAD})} = 400 \text{ V}$

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$I_{L(\text{SECONDARY})} = \frac{P}{\sqrt{3} V_L \cos \theta}$$

$$= \frac{300\,000}{\sqrt{3} \times 400 \times 0,87}$$

$$= 497,72 \text{ A} \quad (3)$$

3.2.2  $I_{PH} = \frac{I_{LS}}{\sqrt{3}} \sqrt{ }$

$$= \frac{497,72}{\sqrt{3}} \sqrt{ }$$

$$= 287,36 \text{ A} \sqrt{}$$

(3)

3.2.3  $S = \frac{P}{\cos \theta}$

$$= \frac{300\,000}{0,87}$$

$$= 344,83 \text{ kVA}$$

OR

$$S = \sqrt{3} V_L I_L$$

$$= \sqrt{3 \times 400 \times 497,72}$$

$$= 344,83 \text{ kVA}$$

(3)

3.2.4  $S_{\text{PRIMARY}} = S_{\text{SECONDARY}} = 344,83 \text{ kVA}$

$$I_L = \frac{S}{\sqrt{3} V_L}$$

$$= \frac{344,83}{\sqrt{3} \times 6\,000}$$

$$= 33,18 \text{ A}$$

(3)

$$3.2.5 \quad I_{PH} = \frac{I_L}{\sqrt{3}} \\ = \frac{33,18}{\sqrt{3}} \\ = 19,16 \text{ A} \quad (3)$$

- 3.3 • Air blast type (or air ventilated type)  
• Oil filled self-cooled type  
• Oil filled water-cooled type (Any 2 x 1 ✓✓) (2)

## QUESTION 4: THREE-PHASE MOTORS AND STARTERS

- |     |   |                |
|-----|---|----------------|
| 4.1 | <ul style="list-style-type: none"><li>• Rotor ✓</li><li>• Stator ✓</li><li>• Stator windings ✓<br/>(Also accept end-plates)</li></ul>   | (3)            |
| 4.2 | <ul style="list-style-type: none"><li>• When the three-phase supply is connected to the motor, a rotating stator field is generated automatically. ✓</li><li>• This rotating stator field induces a large current in the metal rods of the squirrel cage rotor. ✓</li><li>• These induced currents in the rotor create their own magnetic field. ✓</li><li>• The rotating stator field and the rotor magnetic fields react with each other. ✓</li><li>• A force is exerted between the two fields (called torque) and the rotor starts turning in the same direction as the rotating stator field. ✓</li><li>• As the rotor speed increases, less current is induced in the metal rods of the rotor, because the relative speed between the rotating stator field and the rotor decreases as the rotor speed increases. ✓</li></ul> | (6)            |
| 4.3 | Swap (change) any two phases ✓  | (1)            |
| 4.4 | In the event of a power failure the system will switch off, and will not restart until the system is switched on manually by the operator. ✓✓   | (2)            |
| 4.5 | Once the start button is pressed, ✓ the contactor will energise and the normally open contacts will close, including ✓ the hold-in contact (in parallel with the start button) providing a current path to the contactor coil. ✓<br>The contactor will remain energised until the stop button is pressed, or until the power is removed. ✓  | (4)            |
| 4.6 | <ul style="list-style-type: none"><li>• Continuity/resistance test</li><li>• Insulation resistance between windings</li><li>• Insulation resistance between windings and earth</li><li>• Check for exposed wires</li><li>• Check electrical connections in the terminal box</li></ul>   | (Any 2 x 1 ✓✓) |

$$\begin{aligned}
 4.7 \quad 4.7.1 \quad S &= \frac{P}{\cos \theta} \\
 &= \frac{90\,000}{0,85} \\
 &= 105,88 \text{ kVA}
 \end{aligned} \tag{3}$$


$$\begin{aligned}
 4.7.2 \quad I_L &= \frac{P}{\sqrt{3}V_L \cos \theta} \\
 &= \frac{90\,000}{\sqrt{3} \times 400 \times 0,85} \\
 &= 152,83 \text{ A}
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 4.7.3 \quad \cos \theta &= 0,85 \\
 \theta &= \cos^{-1} 0,85 \\
 &= 31,79^\circ
 \end{aligned} \tag{3}$$

$$\begin{aligned}
 4.7.4 \quad N_S &= \frac{60 \times f}{p} \\
 &= \frac{60 \times 50}{2} \\
 &= 1\,500 \text{ RPM}
 \end{aligned} \tag{4}$$

$$\begin{aligned}
 4.7.5 \quad \text{Slip} &= \frac{N_S - N_R}{N_S} \times 100\% \\
 &= \frac{1\,500 - 1\,400}{1\,500} \times 100 \\
 &= 6,67\%
 \end{aligned} \tag{3}$$

4.8

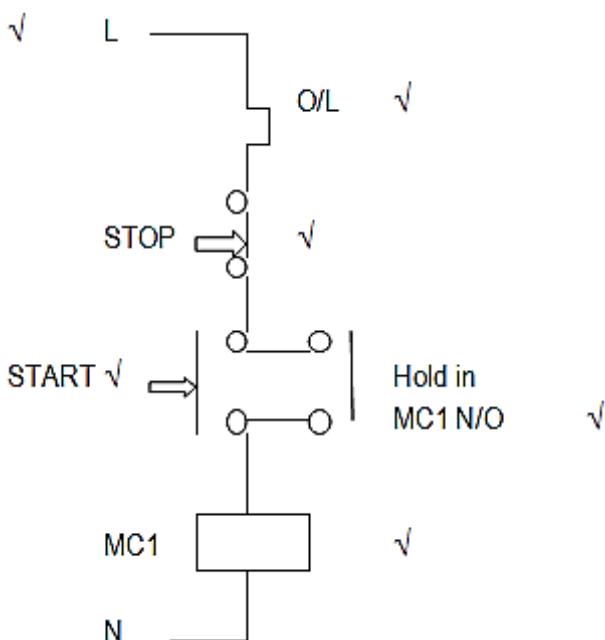(6)  
[40]**QUESTION 5: RCL CIRCUITS**5.1 5.1.1  $X_L$  increases

(1)

5.1.2  $X_C$  decreases

(1)

5.2  $X_L = X_C$ 

Z is at minimum

 $Z = R$ 

I is at maximum

 $\cos \theta = 1$  $\theta = 0^\circ$ 

(Any 2 x 1 ✓✓) (2)

5.3 5.3.1  $I_R = \frac{V_S}{R} = \frac{100}{50} = 2 \text{ A}$

(3)

5.3.2  $I_L = \frac{V_S}{X_L} = \frac{100}{31.42} = 3,183 \text{ A}$

(3)

$$\begin{aligned}
 5.3.3 \quad I_C - I_L &= \sqrt{I_T^2 - I_R^2} \\
 I_C &= \sqrt{I_T^2 - I_R^2 + I_L^2} \\
 &= \sqrt{4,6^2 - 2^2 + 3,183^2} \\
 &= 7,325 \text{ A}
 \end{aligned}$$

(4)

$$5.3.4 \quad \frac{1}{2\pi f c} = \frac{V_s}{I_c}$$

$$X_C = \frac{100}{7325} \quad \checkmark \quad = 13,65 \Omega \quad \checkmark$$

$$C = \frac{1}{2\pi f X_C} \quad \checkmark$$

$$C = \frac{1}{2\pi \times 50 \times 13,65}$$

$$= 233 \mu\text{F}$$

(6)

[20]

## QUESTION 6: LOGIC




6.2



normally open contact ✓



normally closed contact ✓

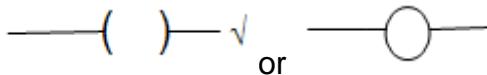

output ✓


(6)

- 6.3

  - Very compact solid state device that is relatively small
  - Uses about 10% of the amount of energy of a relay system
  - Long life and less maintenance
  - Less expensive/Economical
  - No moving parts, therefore more reliable
  - Easy to change the program
  - Fast response

(Any 2 x 1 ✓✓) (2)

6.4

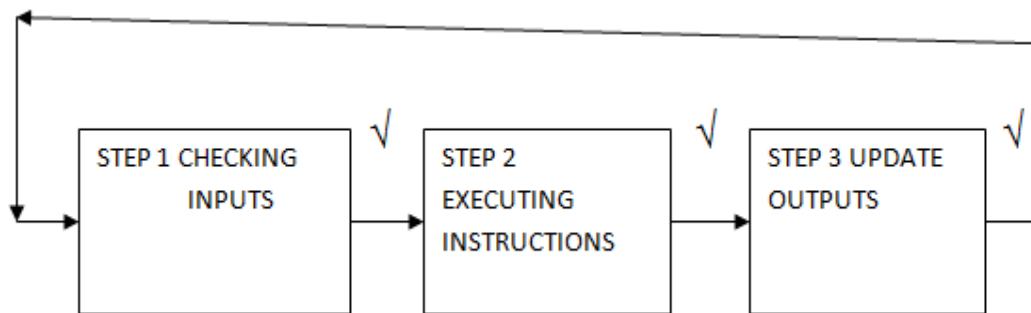

STEP 1: The PLC reads the inputs via the input interface ✓

STEP 2: The PLC will now look at the first instruction in the program and execute it ✓

STEP 3: After the execution of the first instruction all the outputs will now be updated accordingly ✓

After step 3 the PLC will return to step 1 and repeat the process. ✓

(8)

6.5

6.5.1

SENSOR A	SENSOR B	SENSOR C	OUTPUT
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ✓
1	0	0	0
1	0	1	1 ✓
1	1	0	1 ✓
1	1	1	1 ✓

(4)

6.5.2  $F = ABC + ABC + ABC + ABC$  (2 marks are awarded for the correct interpretation from the truth table in QUESTION 6.5.1, otherwise 0) ✓✓

(2)

6.5.3


A

		BC			
		00	01	11	10
0	0	0	0	1	0
	1	0	1	1	1

✓ for correctly drawing the map;  
✓ for correctly entering logic levels


✓ grouping  $\bar{A}BC$  and  $ABC$ ✓ grouping  $A\bar{B}C$  and  $ABC$ ✓ grouping  $ABC$  and  $AB\bar{C}$ SIMPLIFICATION  $F = AB + AC + BC$  ✓

6.5.4

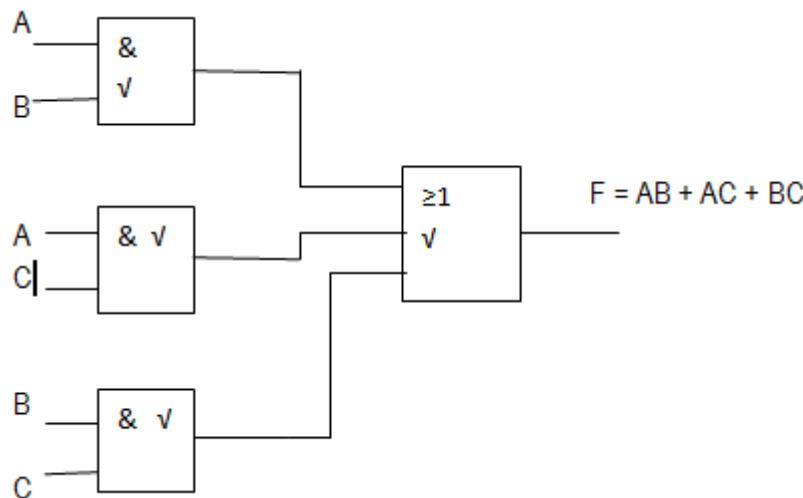

(4)

6.5.5

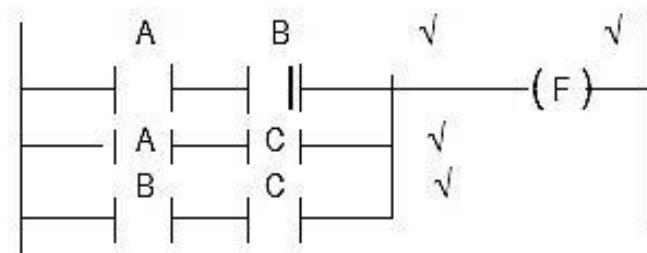(4)  
[40]**QUESTION 7: AMPLIFIERS**


- 7.1
- Infinite open loop gain
  - Infinite Bandwidth
  - Infinite input impedance
  - Output impedance = 0
  - Infinite common mode rejection ratio
  - Very high stability

(Any 3 x 1 ✓✓✓) (3)

7.2 7.2.1 Open loop gain in OP-AMPS means that there is no feedback resistor between the output and the inverting input. ✓✓ (2)

7.2.2 Unwanted signals, such as interference ✓ might appear at the inverting and non-inverting inputs of the op-amp ✓ are not amplified. ✓ (3)

7.3

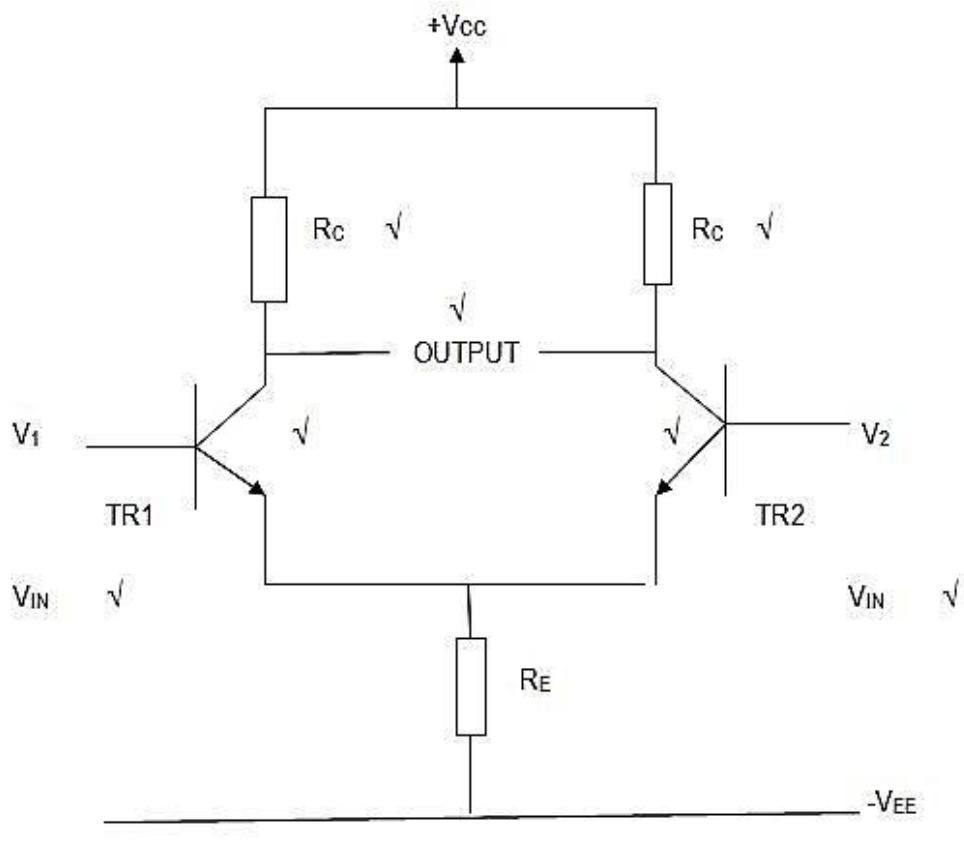

(7)

7.4 When a portion of the output signal is fed back to the input 180° out of phase with the input signal. ✓✓ (2)

7.5

- Increase the bandwidth of the amplifier ✓
- Increases the stability of the amplifier ✓
- Reduces distortion and noise ✓

 (3)


7.6 7.6.1 Summing amplifier ✓ (1)

7.6.2 Audio mixer ✓ (1)

$$V_{OUT} = R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \checkmark$$

$$= -10 \text{ k} \left( \frac{0,2}{1\text{k}} + \frac{0,3}{1\text{k}} + \frac{0,5}{1\text{k}} \right) \checkmark$$

$$= -10 \text{ V} \checkmark$$

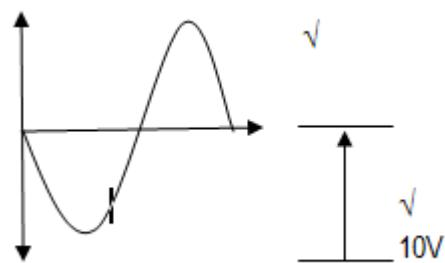

(5)

7.7 7.7.1 Hartley oscillator ✓

(1)


$$7.7.2 f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 220 \times 10^{-9}}}$$

$$= 3\ 393 \text{ Hz}$$

(3)

7.8 7.8.1


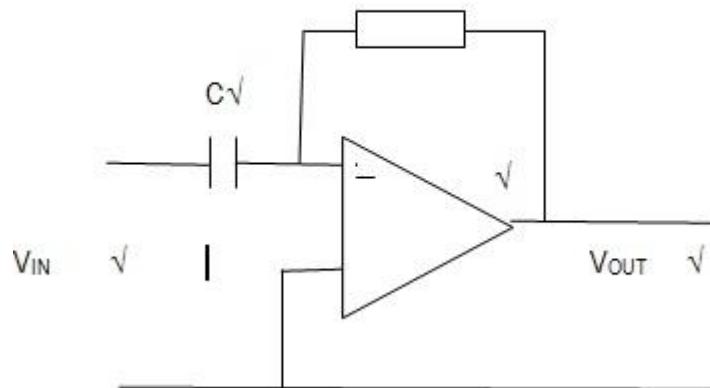
 $R_F$  ✓

(5)

7.8.2 Monitoring the rate of temperature change in a furnace. ✓✓


(2)

7.8.3

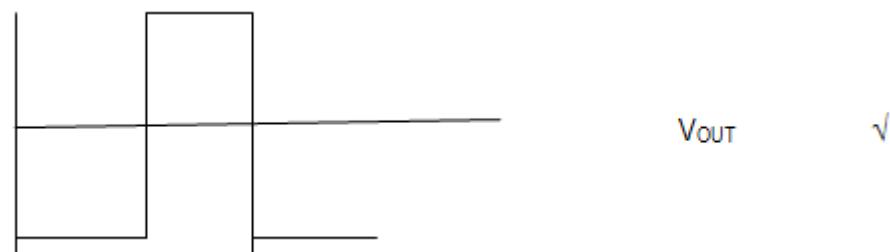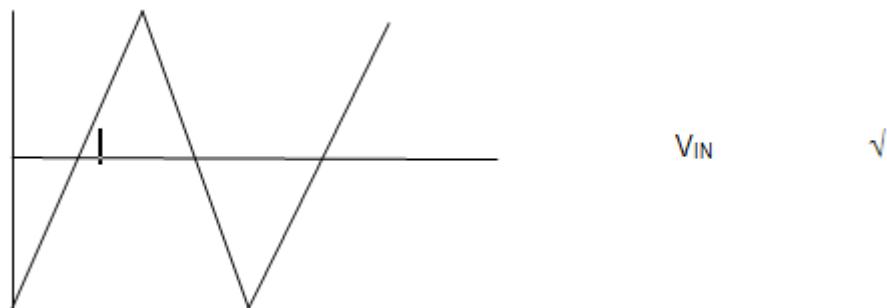

(2)

7.9 7.9.1

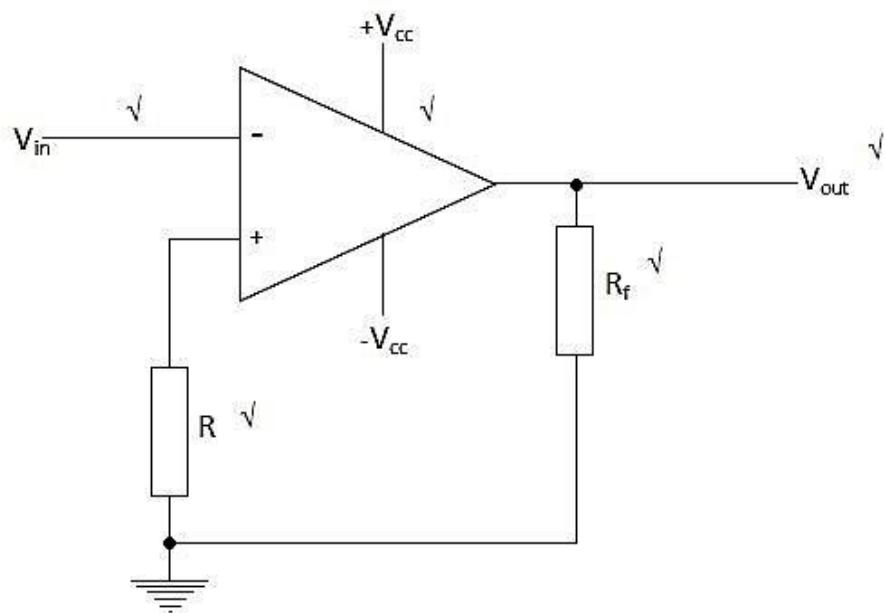

(5)

7.9.2

- Voltage sensitive switch
- Have two fixed trigger values (voltages)
- Supplies a digital output
- Output frequency is the same as input frequency
- Used as a wave shaper

(Any 3 x 1 ✓✓✓) (3)

7.9.3

- Function generators ✓
- Digital counters ✓

(2)

[50]

**TOTAL: 200**

TOTAL: 200


[50]

(2)

(3)



- Digitale teller ✓
- Funksiegenerators ✓

(5)

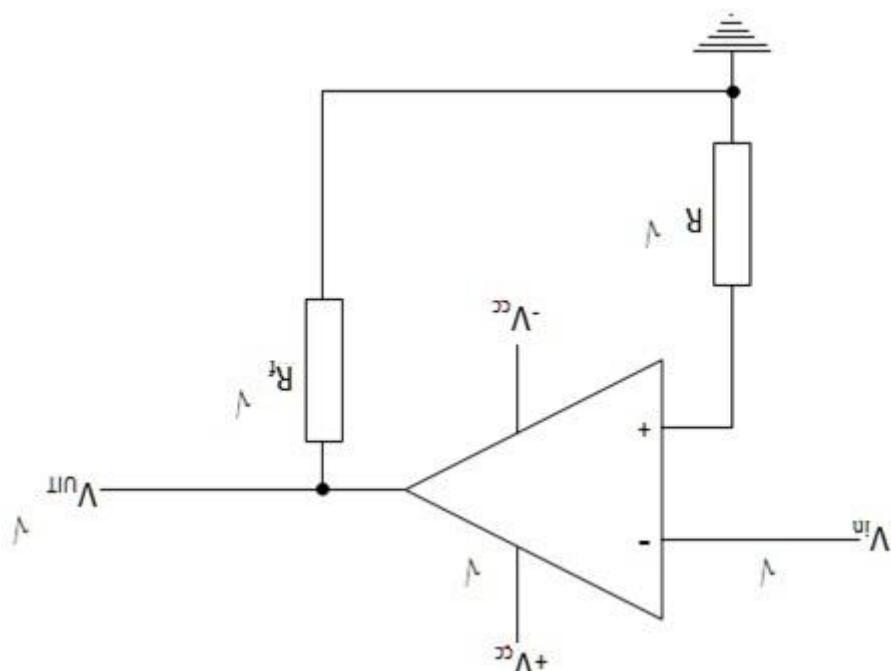

7.9.1

(2)

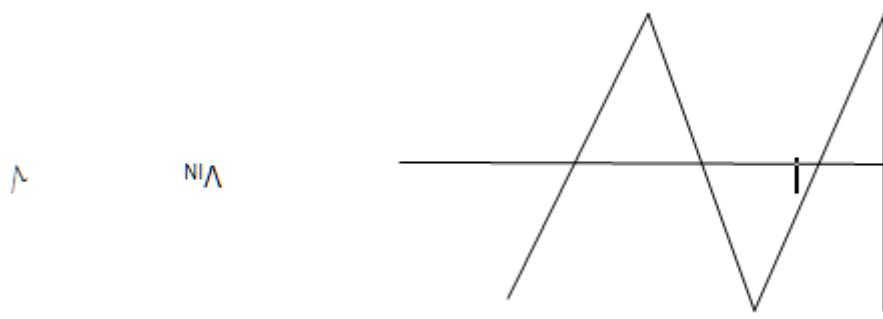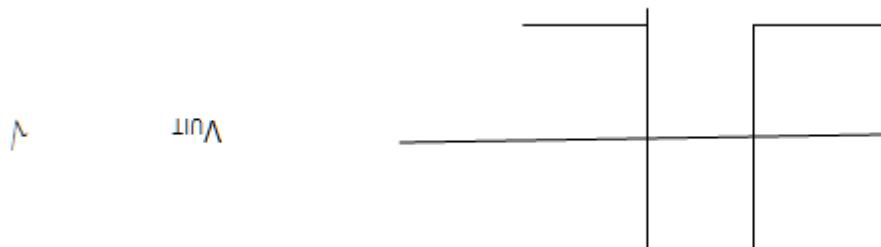


7.8.3

(2)

7.8.2 Monitorring van die tempo van temperatuurverandering in 'n hoogond.

(5)

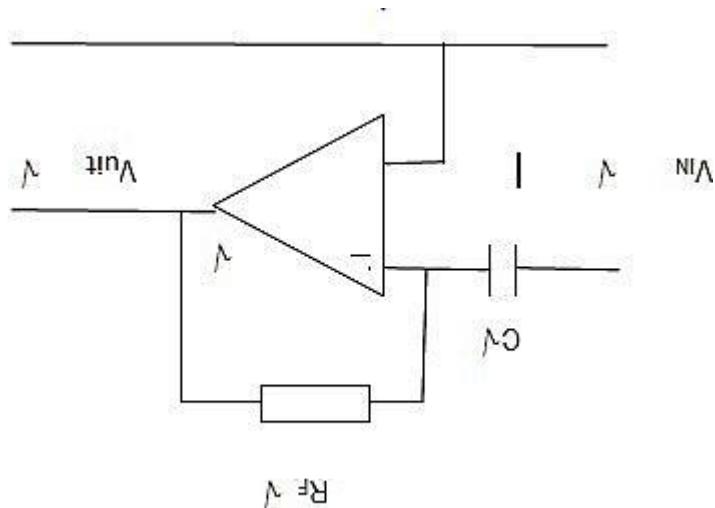

7.8.1

7.8.1

(3)

$$= 3393 \text{ Hz}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{2\pi\sqrt{10 \times 10^{-3} \times 220 \times 10^{-9}}}{1} \text{ Hz}$$


7.7.2

7.7.1

(1)

Hartley-oscillerdeer

(5)

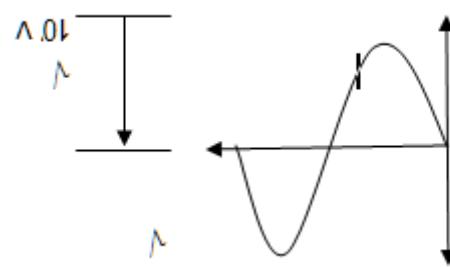

$$= -10V \quad \checkmark$$

$$= -10k \left( \frac{1}{0.2} + \frac{1}{0.3} + \frac{1}{0.5} \right) V$$

$$7.6.3 \quad V_{UIT} = R_F \left( \frac{R_1}{V_1} + \frac{R_2}{V_2} + \frac{R_3}{V_3} \right) V$$

(1)

7.6.2 Oudionemengerv  $\checkmark$ 

(1)

7.6.1 Sommeerversterker  $\checkmark$ 


(3)

7.5 • Vermindert verwringing en geras.  $\checkmark$ • Verhoogde stabilitet.  $\checkmark$ • Toename in bandwijdte van de versterker.  $\checkmark$ 

(2)

7.4 Wanneer h deel van die uitsetein  $180^\circ$  uit fase met die insetein terugvorder word.  $\checkmark$ 

(7)

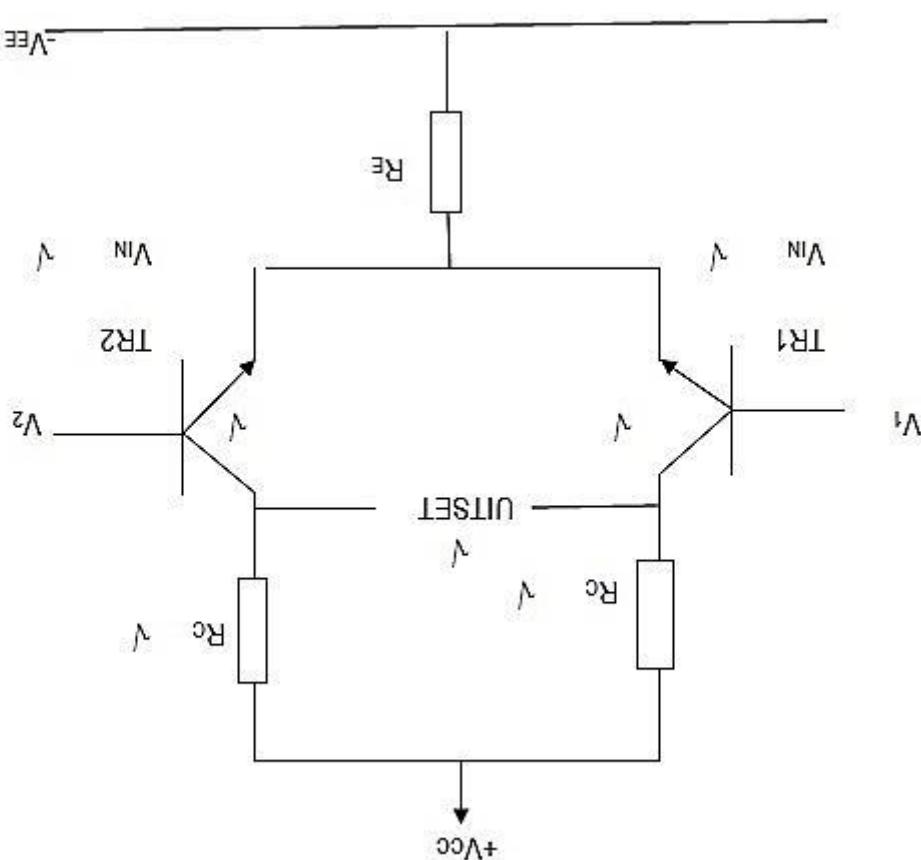

7.3

(3)

7.2.2 Ongewenste seine soos stuurings  $\checkmark$  wat by die omkeer en nie-omkeerinsette  $\checkmark$  verskyн, sal nie versterk word nie.  $\checkmark$ 

(2)


7.2.1 Opp lus wins by OP-AMPS beteken geen terugkopplewewerstand

tussen uitset en omkeerinset.  $\checkmark$


- Oneindige oop lus wins  
• Oneindige bandwydte  
• Oneindige insetimpedansie  
• Uitsetimpedansie = 0  
• Oneindige gemeneeskaplike modulusverperijsverhouding  
• Baie hoe stabilitet  
(Enigte 3 vvw) (3)

VRAG 7: VERSTERKERS

[40]  
(4)

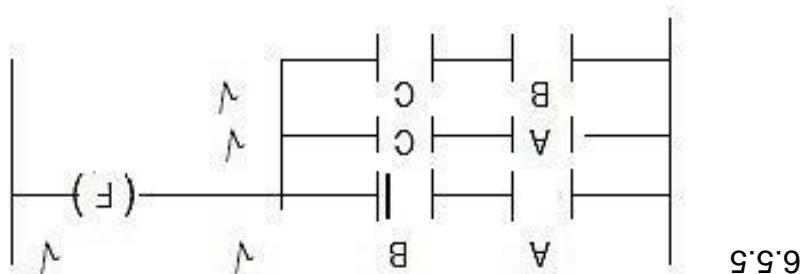

(4)

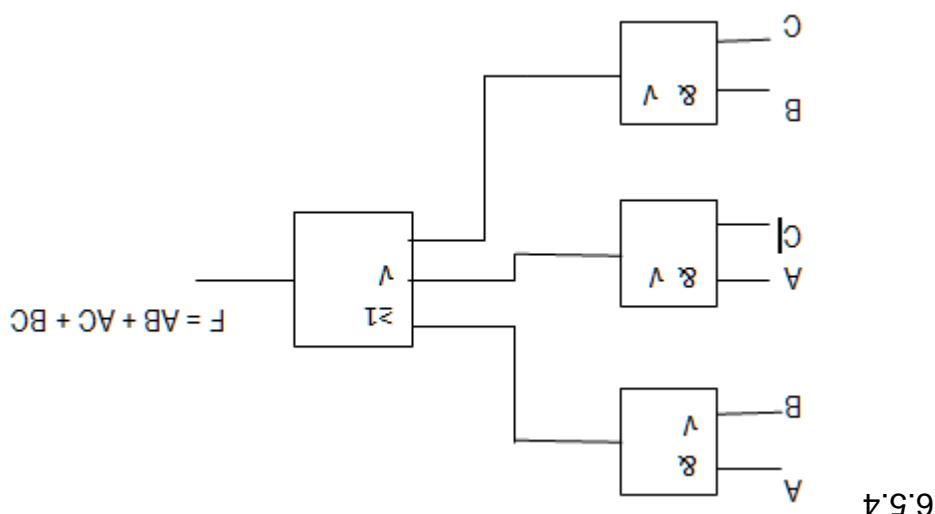

VEREENVOUDIGING  $F = AB + AC + BC \vee$   
groepenring  $ABC$  en  $ABC$   $\wedge$   
groepenring  $ABC$  en  $ABC$   $\wedge$

1	1	1	0
0	1	0	0
10	01	11	00

- ✓ korrekte inset van logikaalake
- ✓ korrekte tekening van kaart

BC

6.5.3 A

(2)

6.5.2  $F = ABC + \bar{A}BC + ABC + \bar{A}\bar{B}C$  (2 punte word gegee vir die korrekte interpretasie van die waarheidsstabel in VRAG 6.5.1; indien nie reg nie dan 0) ✓✓  
 interpreasie van die waarheidsstabel in VRAG 6.5.1; indien nie reg

(4)

	SENSOR A	SENSOR B	SENSOR C	UITSET
1	1	1	1	1 ✓
1	1	1	0	1 ✓
1	0	1	1	1 ✓
1	0	0	0	0
1	0	1	1	1 ✓
0	1	0	0	0
0	0	1	1	0
0	0	0	0	0
0	0	0	0	0


(8)

Na step 3 sal die PLB weer by step 1 begin en die proses herhaal. ✓

STAP 3: Na uitvoering van die eerste instruksie sal alle insette dienoordeunkomstig opgedateer word ✓

STAP 2: Die PLB sal eerst na die eerste instruksie in die program kyk en dit uitvoer ✓

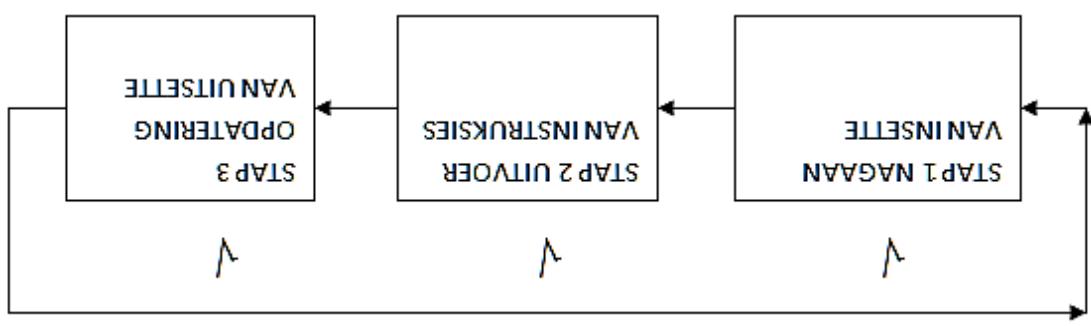STAP 1: Die PLB lees die insette deur die inset-koppelvlak ✓



6.4

6.3 (2) (Enigste 2 x 1 ✓)

- PLB' e is vastestand-toestelle wat relatief klein is
- Gebruik ongeveer 10% van die krag wat rele-logika gebruik
- Hou laank en minder instantandhouding
- Meer bekostigbaar/ekonomies
- Geen bewegende onderdele, gevouliglik meer betroubaar.
- Maklik om die program te verander
- Vinnige reaksieyd

(6)



normalweg geslotte kontak ✓



normalweg oop kontak ✓



6.2

(4)

- Kragtoevoer ✓
- Inset/Uitset-module ✓
- Verwerker ✓
- Programmeringstoestel ✓

**VRAG 6: LOGIKA**[20]  
(6)

$$5.3.4 \quad \frac{1}{V_s} = \frac{2\pi f_c}{I_C}$$

$$X_C = \frac{100}{7.325} \quad \checkmark \quad = 13,65 \Omega$$

$$C = \frac{2\pi f X_C}{1}$$

$$C = \frac{2\pi f C}{1}$$

$$c = \frac{2\pi \times 50 \times 13,65}{1}$$

$$= 233 \mu F$$

(4)

$$= 7,325 \text{ A}$$

$$= \sqrt{4,6^2 - 2^2 + 3,183}$$

$$I_C = \sqrt{I_T^2 - I_R^2 + I_L}$$

$$I_C - I_L = \sqrt{I_T^2 - I_R^2}$$

5.3.3

(3)

$$I_L = \frac{V_s}{X_L} = \frac{31,42}{100} = 3,183 \text{ A}$$

(3)

$$I_R = \frac{V_s}{R} = \frac{50}{100} = 2 \text{ A}$$

(2)

$$\theta = 0^\circ \quad (\text{Enigte } 2 \times 1 \text{ V})$$

$$\cos \theta = 1$$

Is by maksimum

$$Z = R$$

Z is minimum

$$X_L = X_C$$

5.2

(1)

$$X_C \text{ daal}$$


(1)

$$5.1.1 \quad X_L \text{ verhoog}$$

## VRAAG 5: RLC-KRINGE

(6)

[40]

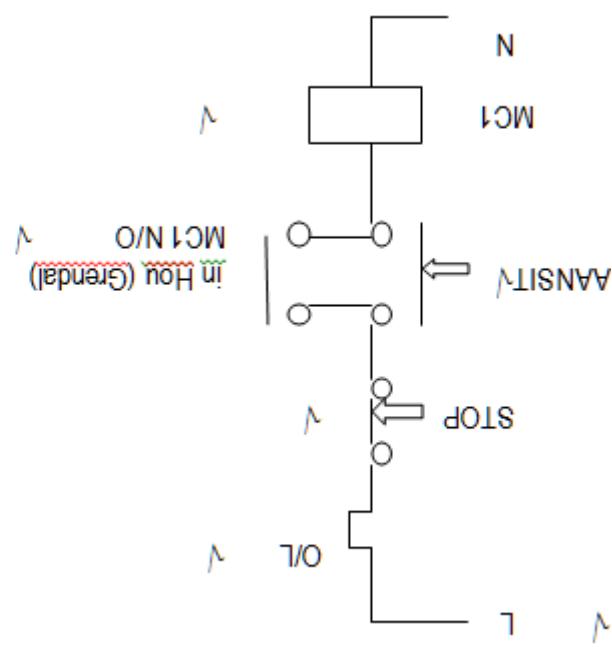

4.8

(3)

$$4.7.5 \quad Gip = \frac{N_s - N_r}{N_s} \times 100\% = \frac{1500 - 1400}{1500} \times 100 = 6,67\%$$

(4)

$$4.7.4 \quad N_s = \frac{P}{f} = \frac{60 \times 2}{60 \times 50} = 1500 \text{ OPM}$$

(3)

$$4.7.3 \quad \cos \theta = 0,85 \quad \theta = \cos^{-1} 0,85 = 31,79^\circ$$

(3)

$$4.7.2 \quad I_L = \frac{\sqrt{3} V_L \cos \theta}{P} = \frac{\sqrt{3} \times 400 \times 0,85}{90000} = 152,83 \text{ A}$$

(3)

$$4.7.1 \quad S = \frac{P}{\cos \theta} = \frac{90000}{0,85} = 105,88 \text{ kVA}$$

- 4.6 • Kontinuïteit/weerstandstoets (Enigte 2 x 1 v/a) (2)
- 4.5 • Wanneer die aansitskakelar gedruk word, sal die spoei van die kontaktor bekrag word en die normale oop kontakte sal sluit, insluitende die in-hou kontak wat (in parallel met die aansitskakelar) die stroombaan na die stopknoppie gedruk word, of die toeverg afskakel. ✓ Die kontaktor sal aangeskakel by tot dat die kontaktorspoei voltooi. ✓ Wanneer die aansitskakelar gedruk word, sal die spoei van die kontaktor hand aangeset moet word. ✓
- 4.4 • Indien daar in kragonderekening gevbeur sal die stelsel afskakel. ✓ Wanneer die krag herstel is, sal die stelsel nie self aanskakel nie. Dit sal weer met die stelsel begin wanneer die krag herstel is.
- 4.3 (1) Rull enige twee fasen om. ✓
- 4.3 (6) Mekaar. ✓ Krag word tussen die twee veldes uitgeoefen (dit word wringkrag genoem) en die rotor begin in dieselfde rigting as die rotterende statorende draai. ✓ Namate die rotorspoed toeneem, word minder strooom in die metalstave van die rotor gevleid en die rotorspoed verander het namate die rotorspoed totgeneem het. ✓
- 4.2 • Wanneer die driefase-toeverg aan die motor verbind word, word in hierdie rotterende statorende statorende sy die metalstave van die kourotor en hierdie geïndusseerde stroome in die rotor skep hulle eie rotormagneteese veld. ✓ Indusser h groot strooom daarin. ✓ Die rotterende statorende en die rotormagneteese veld reageer met mekaar. ✓
- 4.1 (3) Rotor ✓ Stator ✓ Statorkleilings ✓ (Aanvaar endplate ook)

#### VRAAG 4: DRIE-FASE MOTORE EN AANSITTERS

- 3.3 • Lug-blas-tipe (of lugventilasie-tipe) (Enigte 2 x 1 v/a) (2) [20]
- 3.2.5  $I_{PH} = \frac{\sqrt{3}}{L} I_L = \frac{\sqrt{3}}{33,18} = 19,16 \text{ A}$

(3)

$$3.2.4 \quad S_{\text{PRIMERE}} = S_{\text{SEKONDERE}} = 344,83 \text{ kVA}$$

$$I_L = \frac{\sqrt{3}V_L}{S}$$

$$\underline{344,83} = \frac{\sqrt{3} \times 6000}{\sqrt{3} \times 6000}$$

$$= 33,18 \text{ A}$$

(3)

$$S = \sqrt{3}V_L I_L$$

$$= \sqrt{3} \times 400 \times 497,72$$

$$= 344,83 \text{ kVA}$$

OF

$$= 344,83 \text{ kVA} \sqrt{}$$

$$= \frac{300000}{0,87} \sqrt{}$$

$$3.2.3 \quad S = \frac{P}{\cos \theta} \sqrt{}$$

(3)

$$I_{PH} = \frac{\sqrt{3}}{Ls} \sqrt{}$$

$$= \frac{\sqrt{3}}{497,72} \sqrt{}$$

$$= 287,36 \text{ A} \sqrt{}$$

(3)

$$3.2.1 \quad V_{L(\text{SEKONDERE})} = V_{L(\text{LAS})} = 400 \text{ V}$$

$$P = \sqrt{3}V_L \cos \theta$$

$$I_{(SEKONDERE)} = \frac{\sqrt{3}V_L \cos \theta}{P}$$

$$= \frac{\sqrt{3} \times 400 \times 0,87}{300000}$$

$$= 497,72 \text{ A}$$

(Enige  $3 \times 1 \text{ VV}$ ) (3)

- Identiese grootte
- Identiese rendement
- Identiese arbeidsfaktor
- Identiese drywingaanslag
- Identiese spannings- en stroombaanlig
- Identiese windingsvrehoudings

### VRAAG 3: DRIE-FASE TRANSFORMATORS

[20]

(3)

(3)

(6)

(Eenige 1 x 2 V)

(Driefase kan in ster of delta gekoppel word.

• Driefase kan in ster of delta gekoppel word.

meer drywing lewer.

• Vir drie- en enkeleffasemotors van soutgeleke fisiese groottes, sal driefase

Driefasemotors het nie bykomende antisitroombane nodig nie.

• Driefasemotors het n heel hoer antisitdrywing.

• Driefasemotors het n hoer arbeidsfaktor.

• Driefasemotors is doeltreffender.

Die las

Driefasemotors het nie bykomende antisitroombane nodig nie.

• Driefasemotors het n heel hoer antisitdrywing.

• Driefasemotors het n hoer arbeidsfaktor.

• Driefasemotors is doeltreffender.

3

(Enigge 1 x 2 VV)

- Lasverspreidling en fase-balansering word moonstlik gemaak.
  - In Neutrale punt is beskikbaar wanneer daar in ster verbind word. Kostenbesparings.
  - Spanmaatse (of triallemaatse) wat nodig is om dunner kabels te steun, verg minder metaal gedurende konstruksie, met geperdraagande bykomende kostenbesparings mee.
  - Laer stroom beteken dat dunner kabels kan gebruik word en dit bring Minder hittie beteken minder hittie.
  - Laer strome beteken minder hittie.
  - Minder hittie beteken minder verliese.
  - Laer stroom beteken minde Kostenbesparings mee.
- Veraspersing- en -transmissieproseses

(Enigge 1 x 2 VV)

- Driefase het twee verbindings opsiës, naamlik ster en delta.
  - Driefase vereis minder instandhouding.
  - Driefase is goedkooper om te genereer.
  - Driefase krag voorstien drywing aan enkel- of driefase-laste.
  - Fase meer drywing oplek.
  - Vir drie- en enkele-aftermatots van soutgelijke fiese groottes, sal drie-
- Driekinkingsproses

(Enigge 3 x 1 VV) (3)

- Windverlies
- Wrywingsverliese
- Sterverliese of kernverliese
- Koperverliese

(Enigge 2 x 1 VV) (2)

- Geopompte oppergring
- Hydroelektries
- Son-energie
- Wind

2.1 (Die varag handel oor metodes wat in Suid-Afrika gebruik word.)

**VRAAG 2: DRIE-FASE WS-OPEKING**

[10]

(5)

- Die druk van hierdie aarpers (klemband) moet periodiek verlig word om te verhoed dat skade aan die weefsel aangeng word. ✓
- Wanneer daar ernstige bloeding is war h groot slagoor afgesny is, kan druk onvoldoende wees en is dit nodig om h aarpers (klemband) te gebruik. ✓
- Hou die bloedingssput, indien moonstlik, bokant die hartvlak. ✓
- Wanneer daar ernstige bloeding is is dit nodig om h aarpers (klemband) te gebruik. ✓
- Wend direkte druk aan, of gebruik 'n drukverband. ✓

1.2 Nee. ✓ Die werker het die reg op privaatheid. ✓ (2)

1.1 In Ongeleuk is h onbeplande, ✓ onbeheerde geboustrukturens ✓ wat deur onveilige optredede en toeslange veroorzaak word. ✓ (3)

**VRAAG 1: BEROPSGESONDHEID EN VEILIGHEID**

---

Hierdie memorandum bestaan uit 13 bladsye.

---

PUNTE: 200

## **ELEKTRIESE TEGNOLOGIE MEMORANDUM**

**SEPTEMBER 2014**

**GRAAD 12**

**SENIOR SERTIFIKAAT  
NASIONALE**

**EASTERN CAPE**  
Province of the  
EDUCATION

